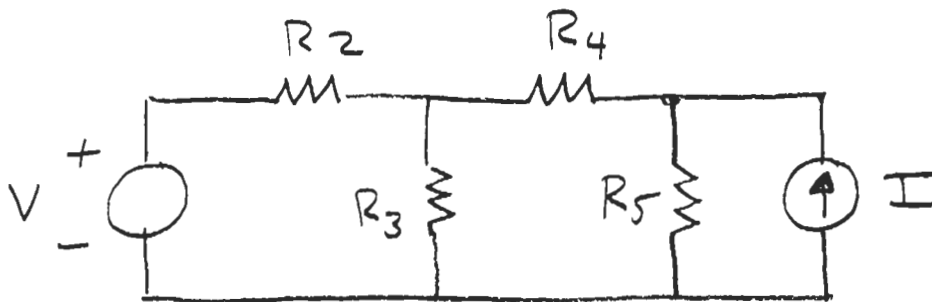


Lecture 54

The Node Method

Consider the network:




This simple network has

6 branch currents
6 branch voltages
12 unknowns

3 (independent) loops
3 (independent) nodes
6 constitutive laws
12 equations

So can solve, but what a mess!
Need an organized way to solve —
the node method!

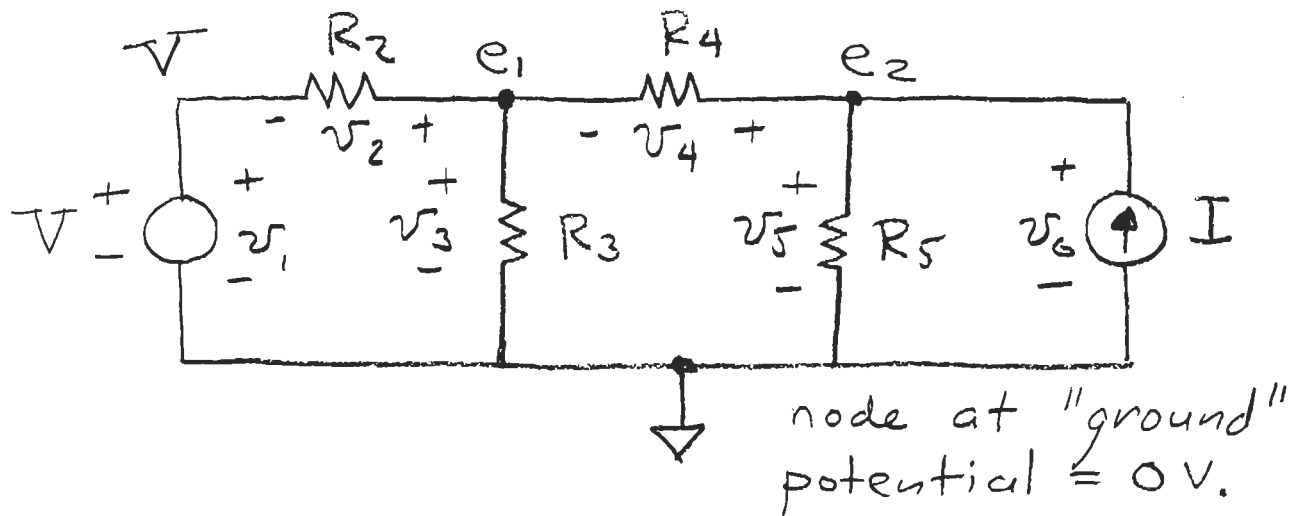Key observation —
KVL holds for networks because
we can assign a potential to
each node, and branch voltages
are just differences in potentials



KVL in center loop:

$$-v_3 - v_4 + v_5$$

$$= -(e_1 - 0) - (e_2 - e_1) + (e_2 - 0)$$

$$= 0$$

So don't have to worry about KVL!

Now apply KCL at nodes.

$$e_1: i_2 + i_3 - i_4 = 0$$

$$\Rightarrow \frac{1}{R_2} (e_1 - V) + \frac{1}{R_3} (e_1 - 0) - \frac{1}{R_4} (e_2 - e_1) = 0$$

Collecting terms:

$$\left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) e_1 - \frac{1}{R_4} e_2 - \frac{1}{R_2} V = 0$$

Let $G = \frac{1}{R}$. ($G = \text{"conductance"}$) Then

$$(G_2 + G_3 + G_4) e_1 - G_4 e_2 = G_2 V$$

[do node method concept test]

At node e_2 , current out of node is

$$\frac{e_2 - e_1}{R_4} + \frac{e_2 - 0}{R_5} - I = 0$$

$$\Rightarrow \left(\frac{1}{R_4} + \frac{1}{R_5} \right) e_2 - \frac{1}{R_4} e_1 = I$$

$$\Rightarrow (G_4 + G_5) e_2 - G_4 e_1 = I$$

So the two equations together are:

$$\begin{cases} (G_2 + G_3 + G_4) e_1 & - G_4 e_2 = G_2 V \\ - G_4 e_1 & + (G_4 + G_5) e_2 = I \end{cases}$$

In matrix form, the equations are:
 sum of conductances connected to e_1 conductance connecting e_1 to e_2

conductance \times Voltage of known source connected to e_1

$$\begin{bmatrix} G_2 + G_3 + G_4 & -G_4 \\ -G_4 & G_4 + G_5 \end{bmatrix} \begin{Bmatrix} e_1 \\ e_2 \end{Bmatrix} = \begin{Bmatrix} G_2 V \\ I \end{Bmatrix}$$

conductance connecting e_2 to e_1 sum of conductances connected to e_2 known source into e_2

Can solve using Cramer's rule or Gaussian elimination:

$$e_1 = \frac{\begin{vmatrix} G_2 V & -G_4 \\ I & G_4 + G_5 \end{vmatrix}}{\begin{vmatrix} G_2 + G_3 + G_4 & -G_4 \\ -G_4 & G_4 + G_5 \end{vmatrix}}$$

$$= \frac{(G_4 + G_5) G_2 V + G_4 I}{(G_4 + G_5)(G_2 + G_3 + G_4) - G_4^2}$$

$$e_2 = \frac{(G_2 + G_3 + G_4)I + G_2 G_4 V}{(G_4 + G_5)(G_2 + G_3 + G_4) - G_4^2}$$

(In a real problem, would be much easier to do numerically than symbolically.)

[second concept test here]