

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.013/ESD.013J Electromagnetics and Applications, Fall 2005

Please use the following citation format:

Markus Zahn, Erich Ippen, and David Staelin, *6.013/ESD.013J Electromagnetics and Applications, Fall 2005*. (Massachusetts Institute of Technology: MIT OpenCourseWare). <http://ocw.mit.edu> (accessed MM DD, YYYY). License: Creative Commons Attribution-Noncommercial-Share Alike.

Note: Please use the actual date you accessed this material in your citation.

For more information about citing these materials or our Terms of Use, visit:  
<http://ocw.mit.edu/terms>

Problem Set #10  
 Fall Term 2005

Issued: 11/22/05  
 Due: 11/30/05


Suggested Reading Assignment: Lecture Notes 18

Problem 10.1


A magnetohydrodynamic (MHD) machine of height  $s$  and width  $a$  is placed within a magnetic circuit. The fluid moving at velocity  $V$  out of the paper obeys Ohm's law

$$\vec{J} = \sigma(\vec{E} + \vec{V} \times \vec{B})$$

and has magnetic permeability  $\mu_o$ .

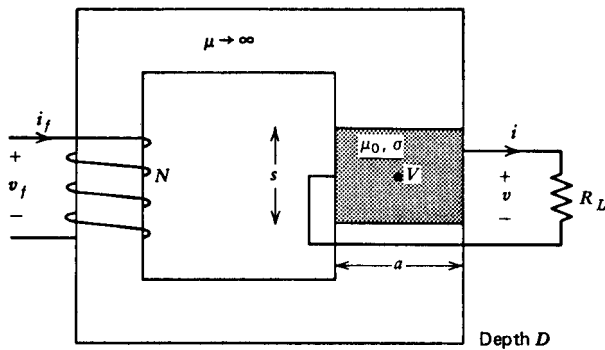

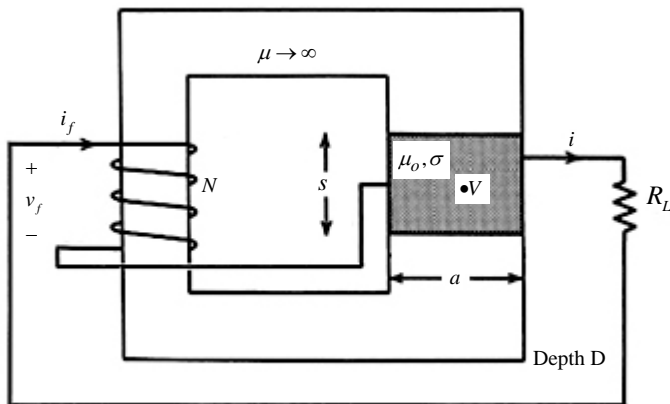- (a) A constant dc current  $i_f = I_0$  is applied to the  $N$  turn coil. What is the magnetic field  $\vec{B}$  in the MHD machine?
- (b) What is the voltage  $v$  across the load resistor  $R_L$ ?




- (c) The MHD machine and load resistor  $R_L$  are now connected in series with the  $N$  turn coil that has a resistance  $R_f$  as shown in the figure to the left. No current is applied but at  $t = 0$  noise causes a small current so that  $i_f(t = 0) = i(t = 0) = I_0$ . Neglecting magnetic saturation of the iron core of the magnetic current, what is  $i_f(t)$  for  $t \geq 0$ ?
- (d) Under what conditions is  $i_f(t)$  unbounded as  $t \rightarrow \infty$ ? Such a system is called DC self-excited.

Adapted from Problem 6.20 in *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.
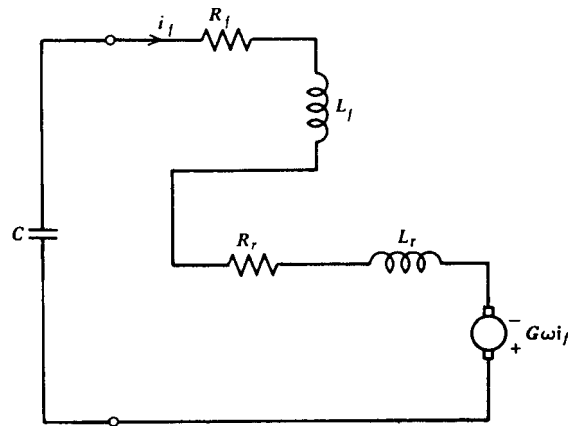
### Problem 10.2

The field winding of a homopolar generator is connected in series with the rotor terminals through a capacitor  $C$  as shown in the equivalent circuit below. The rotor is turned at constant speed  $\omega$ .



- For what minimum value of rotor speed is the system self-excited?
- For the self-excited condition of (a) what range of values of  $C$  will result in dc self-excitation or in ac self-excitation?
- What is the frequency for ac self-excitation?

Problem 6.21 in *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

### Problem 10.3

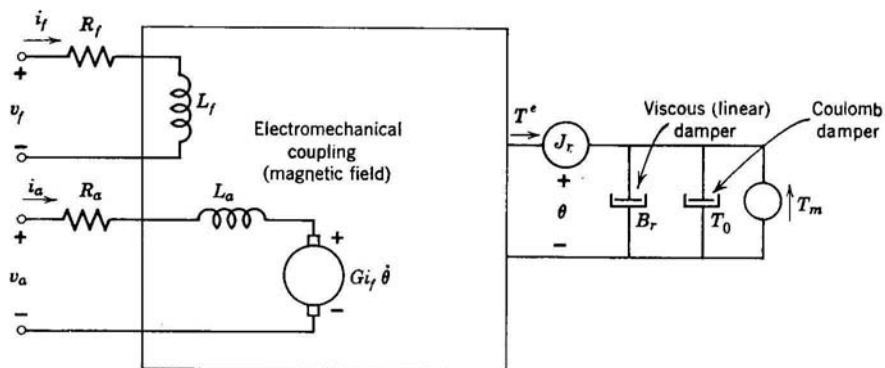


Figure 6.4.5 in *Electromechanical Dynamics*, by Herbert H. Woodson and James R. Melcher, 1968.

The electromechanical equivalent circuit of a commutator machine is shown above. The field and armature windings can be connected in parallel (shunt excitation) or in series (series excitation) as shown below:

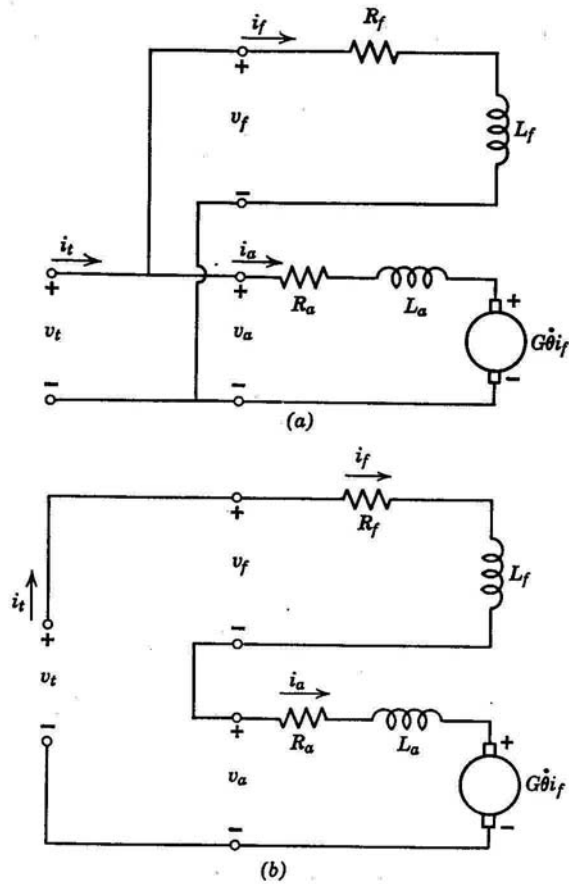


Figure 6.4.9 in *Electromechanical Dynamics*, by Herbert H. Woodson and James R. Melcher, 1968.

The electromagnetic torque on the armature (rotor) with moment of inertia  $J_r$  is  $T^e = G i_f i_a$ .

- A DC voltage source  $V_0$  is connected across the  $v_t$  terminals for shunt and series excitations. In the DC steady state, find the terminal current  $i_t$  and torque  $T^e = G i_f i_a$  as a function of armature angular speed  $\omega = \dot{\theta}$  for shunt and series excitations.
- The voltage source of part (a) that was connected across the  $v_t$  terminals is now removed and is replaced by a load resistor  $R_L$  for shunt and series configurations. Assume that all circuit variables vary as  $e^{st}$  and find natural frequency  $s$  for each configuration. For what rotor speed ( $\omega = \dot{\theta}$ ), direction and magnitude, will the generator be self-excited for each configuration?

**Hint:** The shunt excitation algebra can be involved without some forethought. To simplify the math manipulations for this linear model it is convenient to immediately write the currents  $i_f$  and  $i_a$  as

$$i_f = I_f e^{st}$$

$$i_a = I_a e^{st}$$

Solve for solutions for  $s$  and find unstable roots.