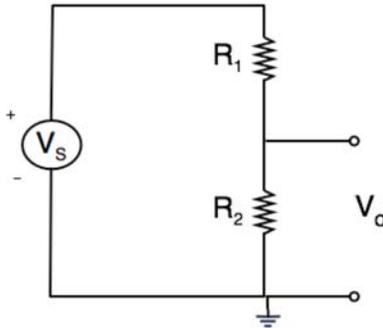


Problem Wk.7.2.2: Resistor Dividers

Part 1: Unloaded

The questions below refer to the following circuit



1. For a given set of values for R_1 and R_2 , if R_2 is then increased, will the voltage V_o increase or decrease? (Enter either *increase* OR *decrease*)


2. If $R_1 = 100$ Ohm and $R_2 = 10,000$ Ohm, *approximately* what is the ratio V_o/V_S ? (Enter a floating point number)

3. If $R_1 = 10,000$ Ohm and $R_2 = 100$ Ohm, *approximately* what is the ratio V_o/V_S ? (Enter a floating point number)

4. If $V_o = 1/5 V_S$ what is the ratio R_1/R_2 ? (Enter a floating point number)

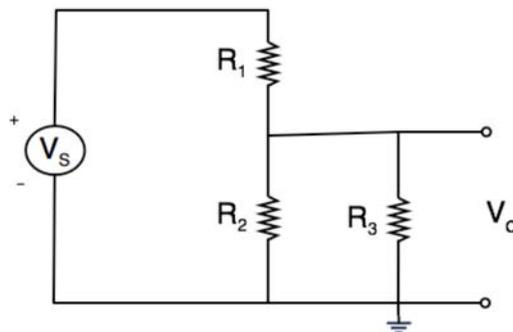Part 2: Loaded

The questions below refer to the following circuit



Note that the only difference between this circuit and the one in the previous part is the addition of R_3 . We are interested in the effect on V_o of adding this resistor. Call the voltage across R_2 when R_3 is not present V_d . Assume R_1 and R_2 are 1000 Ohm.

1. If R_3 has a very high value, say 100,000 Ohm, how does the new value of V_o compare to the value V_d (defined above)? Enter the approximate numerical value of V_o/V_d . (Enter a number with two digits to the right of the decimal point)

2. If R_3 has a very low value, say 10 Ohm, how does the new value of V_o compare to the original value V_d ? Enter the approximate numerical value of V_o/V_d . (Enter a number with two digits to the right of the decimal point)

3. If $R_1 = R_2 = R_3$, how does the new value of V_o compare to the original value V_d ? Enter the approximate numerical value of V_o/V_d . (Enter a number with two digits to the right of the decimal point)

MIT OpenCourseWare
<http://ocw.mit.edu>

6.01SC Introduction to Electrical Engineering and Computer Science
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.