

Low-Power High-Speed Links

Gu-Yeon Wei

Division of Engineering and Applied Sciences

Harvard University


6.976 Guest Lecture, Spring 2003

Outline

- Motivation
- Brief Overview of High-Speed Links
- Design Considerations for Low Power
- DVS Link Design Example
- Summary

Motivation

 - Demand for high bandwidth communications
- Advancements in IC fabrication technology
 - Higher performance
 - More complex functionality
 - Chip I/O becomes performance bottleneck
 - Increasing power consumption
- Network router example




- 10's to 100's of links on a single crosspoint switch
-

High-Speed Links Overview

- High-speed data communication between chips across an impedance controlled channel
 - Shared communication bus (memories)
 - Point-to-point links
- Types of link architectures and implementations
 - Parallel vs. serial
 - Differential vs. single-ended
 - Low-impedance vs. high-impedance driver
 - Transmitter-only vs. receiver-only vs. double termination
- We will focus on point-to-point serial links using differential high-impedance drivers with double termination for network routers
 - Techniques to reduce power applicable to other link types

Link Components

 
- High-speed links consist of 4 main components



- Serializing transmitter driver
- Communication channel
- De-serializing receiver samplers
- Timing recovery



Performance Limitations

- Important to look at performance because higher performance can lead to lower power by trading off performance for energy reduction
- Several factors limit the performance of high-speed links
 - Non-ideal channel characteristics
 - Bandwidth limits of transceiver circuitry
 - Noise from power supply, cross talk, clock jitter, device mismatches, etc.
- Eye diagrams – a qualitative measure of link performance

 


Channel Impairments and ISI

  - One of the dominant causes of eye closure is inter-symbol interference (ISI) due to channel bandwidth limitations
 - Two ways to view channel impairments




Equalization

 - Placing a high-pass filter in the signal path can counter the roll-off effects of the channel
 - Preemphasis or transmit-side equalization is commonly used




Critical Path in Links

 - The critical path in links can be as short as 1~2 gate delays
 - Transmit path




- Receive path

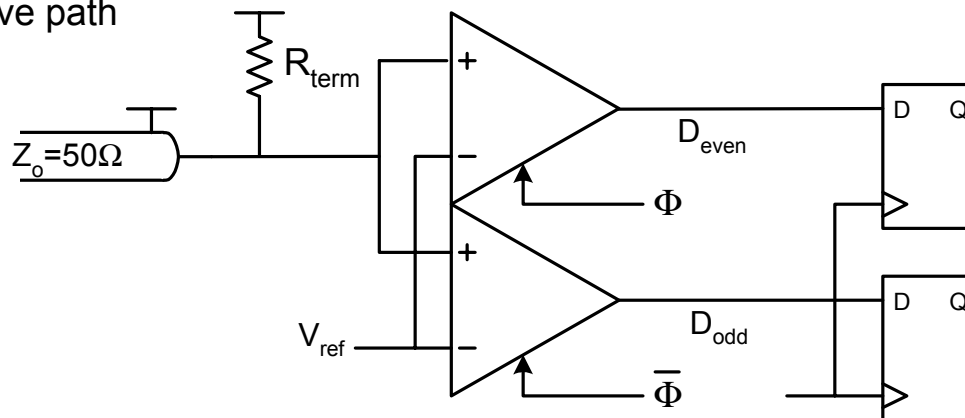

Clock Frequency Limit

 
- While a symbol time can be short, there is a limit to the maximum on-chip clock frequency
 - Must distribute a clock driven by a buffer chain



- Overcome this limitation with parallelism

Parallelism

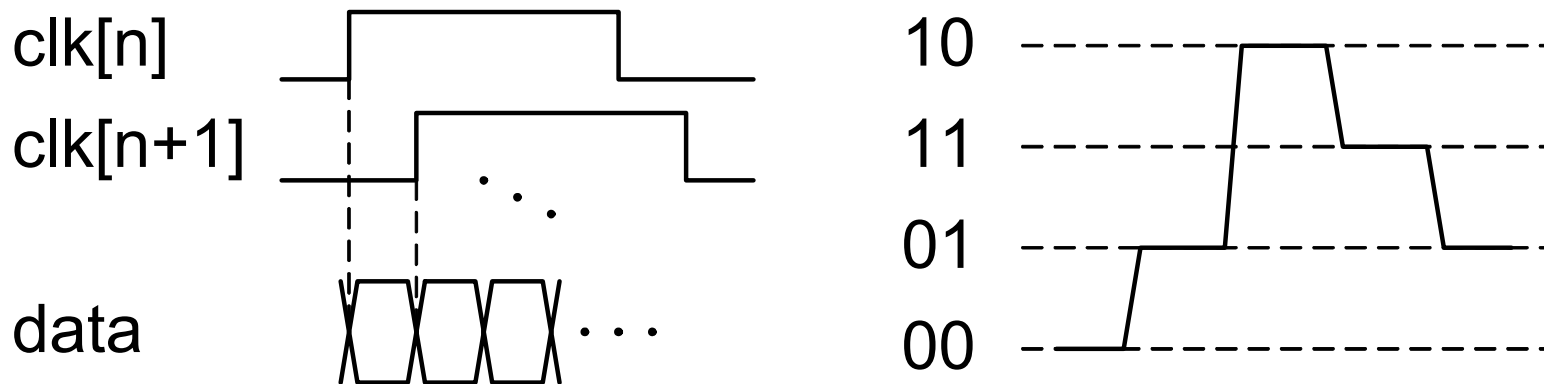- Parallelism can increase bit rate even with limited clock frequency
 - Time-interleaved multiplexing
 - Multi-level signaling



- Some performance issues to be wary of
 - Static timing offsets in multi-phase clock generator (DLL or PLL)
 - Requires higher voltage dynamic range in transmitter and receiver
- Parallelism can also be low power

Sources of Noise


- Power supply noise
 - Translates into voltage and timing uncertainty
- Cross talk
 - Near- and Far-End Cross Talk (NEXT and FEXT)
 - High-frequency coupling
- Clock Jitter
 - Timing uncertainty in transmitted and sampled symbol
 - Probabilistic distribution of timing edges (bounded and unbounded components)
- Device mismatches and systematic offsets
 - Deterministic or systematic variation in timing edges from multi-phase clock generators

Considerations for Low Power

- Low noise → low power
 - Target some signal to noise ratio (SNR)
 - Reducing noise allows for lower signal power
- Trade speed for lower power
 - Reducing bit rate improves SNR
 - Many noise sources are fixed → ratio of timing uncertainty to bit time improves (have longer bit times)
- Let's look at a few design choices for low power
 - Circuit level
 - Architecture level
 - System level

Offset Calibration

 
- Two sets of offsets that can manifest itself as voltage and timing uncertainty to close the eye and may require higher power to overcome them:
 - Multi-phase clock generator timing offsets
 - Receiver input voltage offsets



- Static offsets due to systematic (layout) and random (device) mismatches
 - Calibration enables more timing and voltage margins (i.e., lower noise)

Differential Signaling

 
- Differential communication can lead to a lower power solution
 - Immunity to common mode noise
 - Injects less noise into the supplies
- But aren't there now are two channels that switch? Yes, but...
 - Signal amplitudes can be smaller on both channels
 - Alternative is pseudo-differential signaling but needs a reference voltage which can be noisy and require larger V_{swing}



- What does it cost?
 - Requires two pins per link


Signal Multiplexing

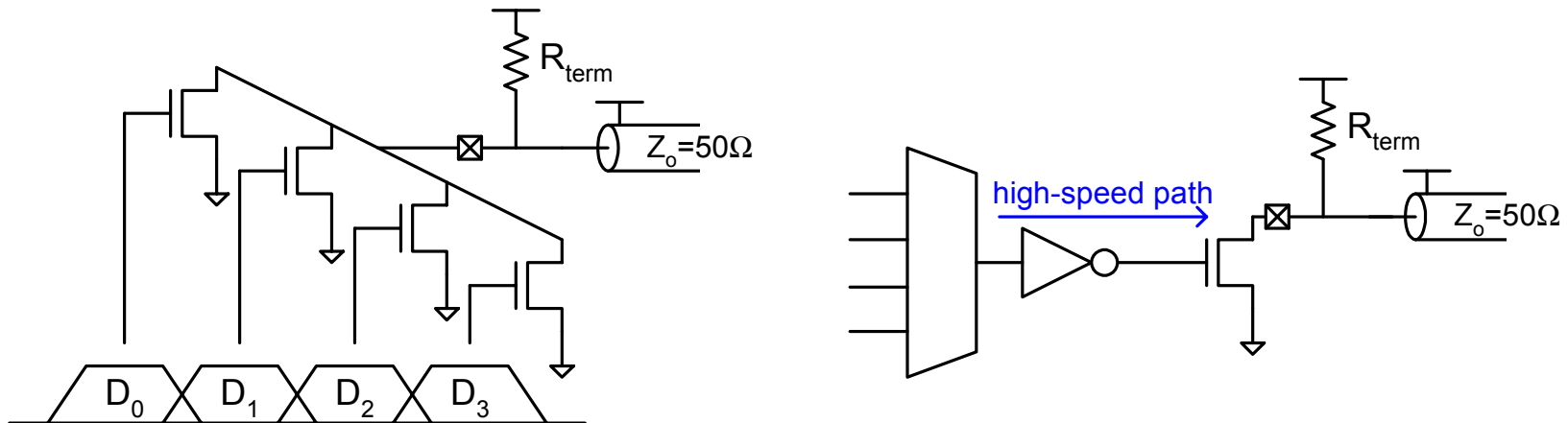- There are different options for choosing where to combine pulses to create sub-clock period symbols
 - Combine at the final transmitter stage vs. farther up stream



- C_{load} for the clocks higher when combined at the final transmitter vs.
 - Need faster signal path after the multiplexer
- Best choice depends on implementation (see Zerbe, ISSCC2003)

Multiplexing

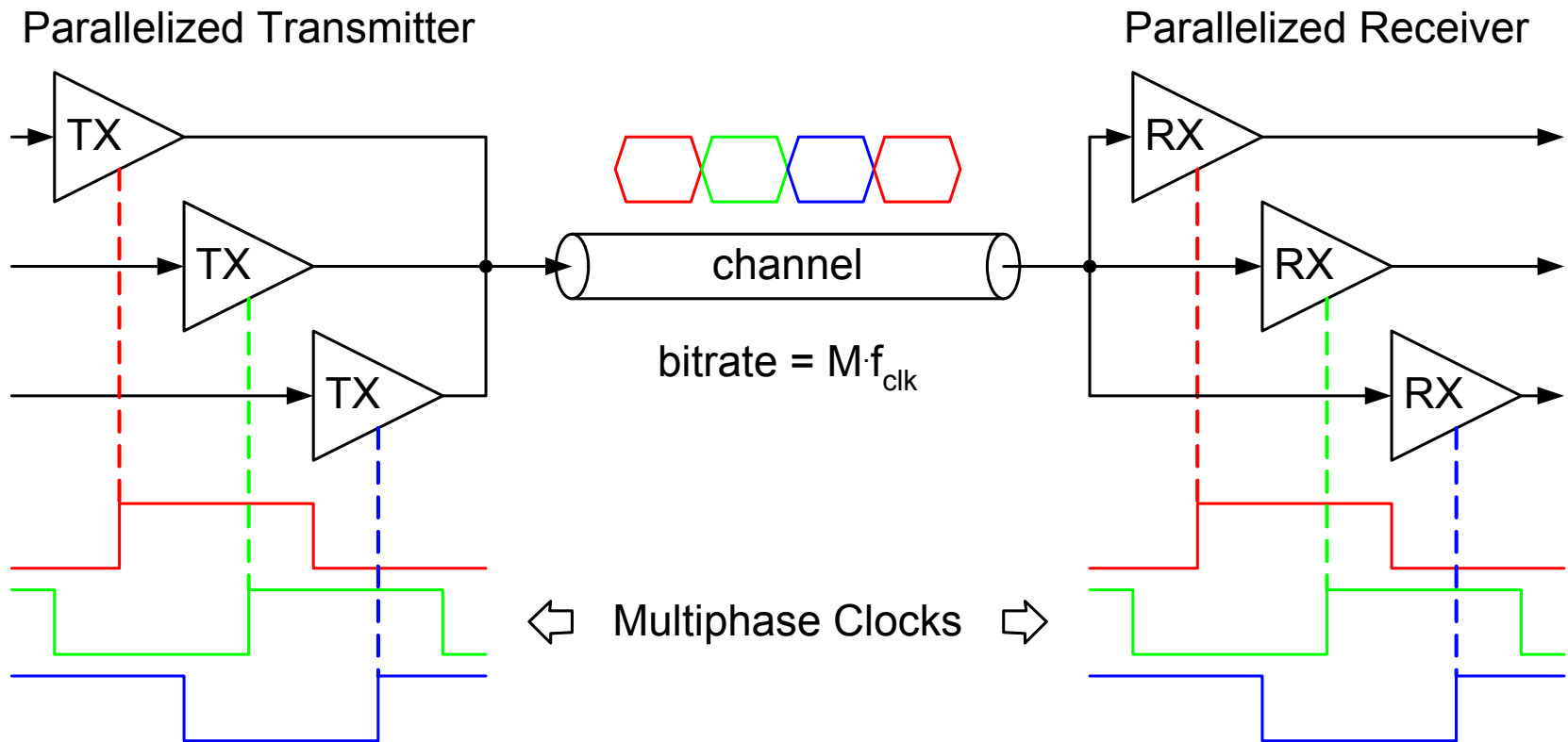

Multiplexing = Low Power?

With M:1 multiplexing, $f_{\text{CLK}} = \text{bit rate}/M$


- Power = $M \cdot C V^2 \cdot f = M \cdot C V^2 \cdot (\text{BR}/M) = C \cdot V^2 \cdot \text{BR}$
- With fixed supply, power does not vary with M

But wait, at lower frequencies, I can lower voltage!

- With lower supply voltage ($V \propto f_{\text{CLK}} = \text{BR}/M$),
- Power decreases as $\propto 1/M^2$!

Power vs. M

 - Larger M
 - ⇒ Can reduce voltage
 - ⇒ Lower power
 - ⇒ Less accurate timing
 - static phase offsets
 - jitter
- Cannot make M arbitrarily large b/c there is a lower limit to V_{dd}
- Choice: M= 4~6




This begs the questions... What if we make V_{dd} adaptive w/ f_{CLK} ?

DVS Links

- Dynamic Voltage Scaling (DVS)
 - Technique first introduced for digital systems (e.g., uP, DSP chips)
 - Lot's of work done in both academia and industry (e.g., Intel, Transmeta)
 - Allows trade off between speed and power
- Let's investigate DVS for high-speed links
 - Motivation and potential benefits
 - Design example from Dr. Jaeha Kim (ISSCC2002, JSSC2002, PhD thesis 2002)


DVS Links

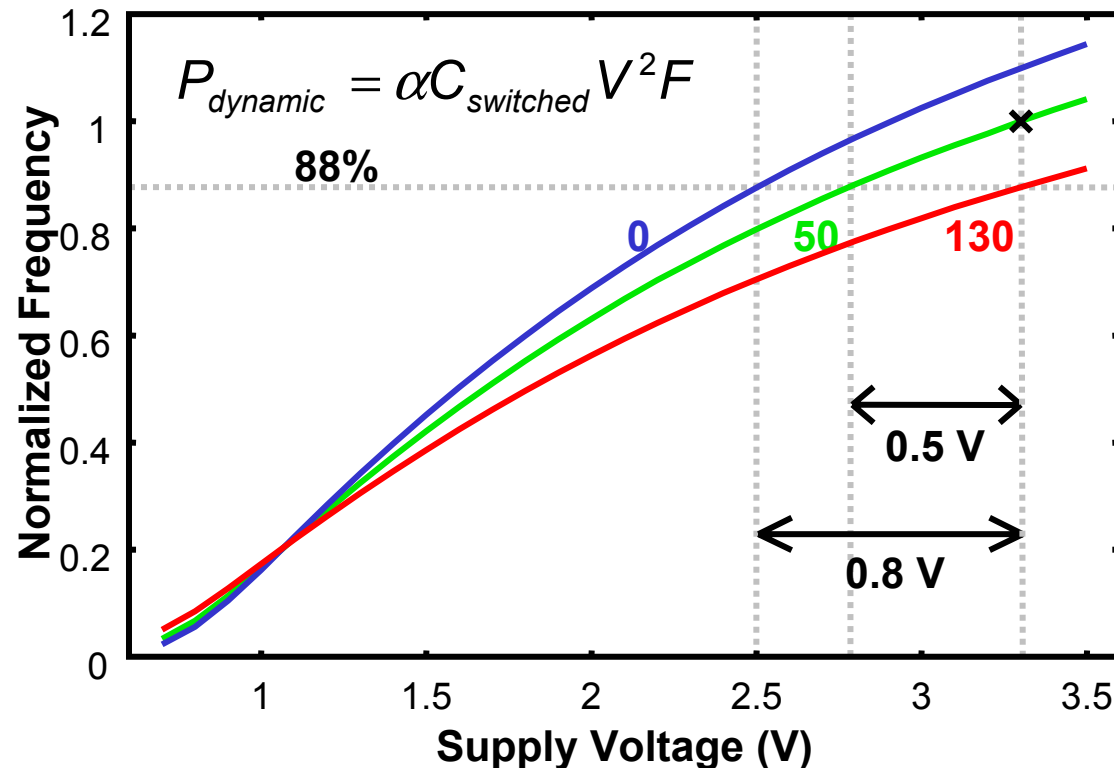- Dynamic Voltage Scaling (DVS) can reduce power consumption in two ways
 - 1) Digital circuits operate at their most energy-efficient point in the presence of PVT variations by eliminating extra performance margins




Trade Performance for Energy Savings

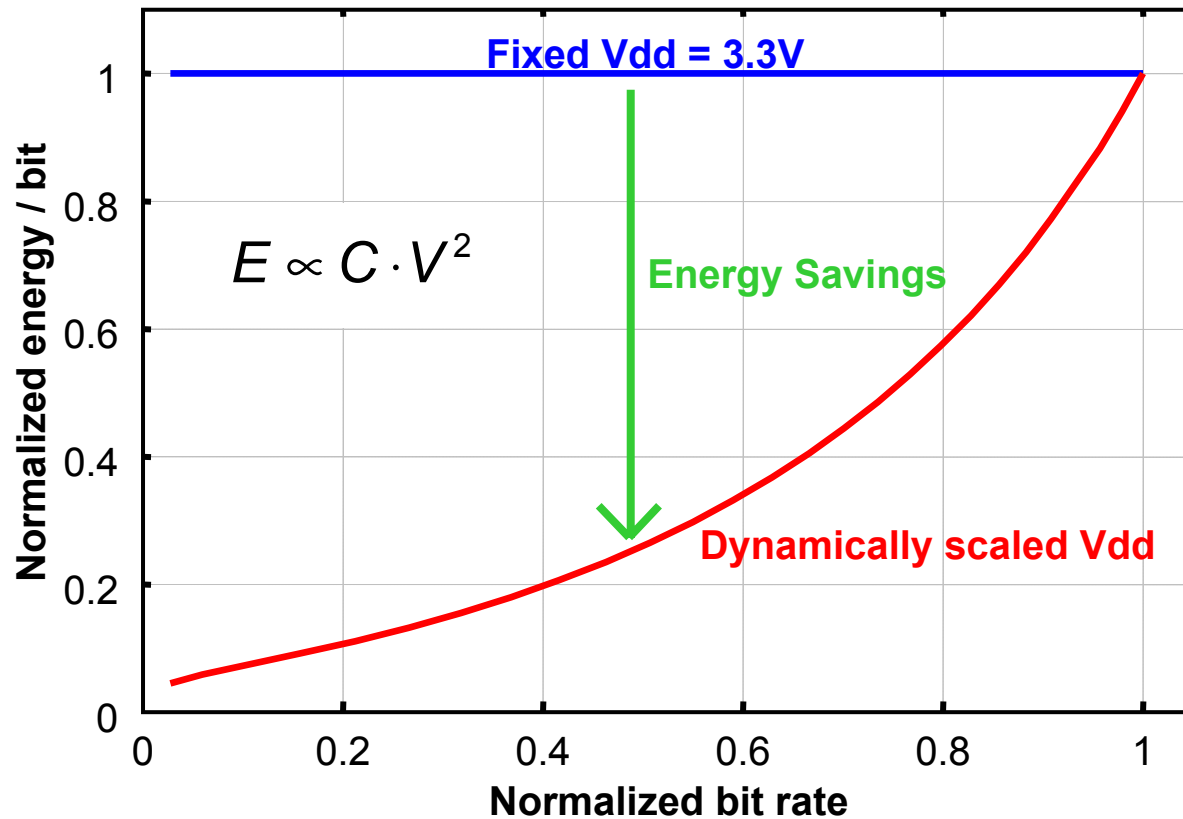- 2) DVS enables trade off between performance and energy
- Reducing frequency alone reduces power but not energy per bit





DVS Link Components

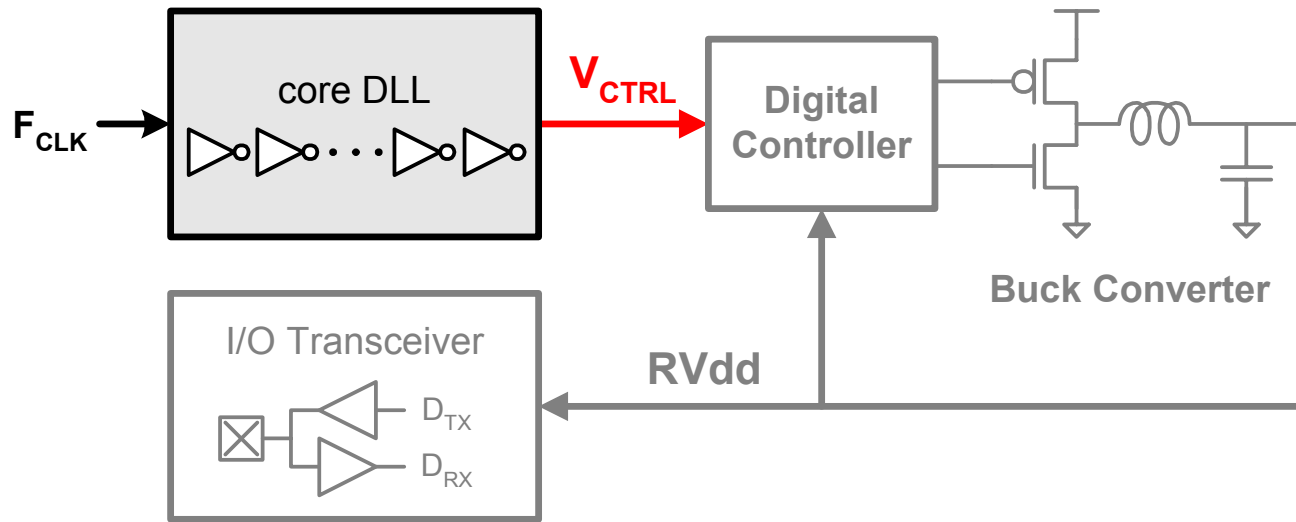- DVS links require two additional components
 - Mechanism to measure circuit critical path to appropriately adjust voltage with respect to frequency
 - Use an on-chip performance monitor circuit (inverter delay elements of core DLL)
 - Efficient supply-voltage regulator (buck converter)
- Overall Block diagram (Wei *et al*, ISSCC2000)



Adaptive Receiver Filter

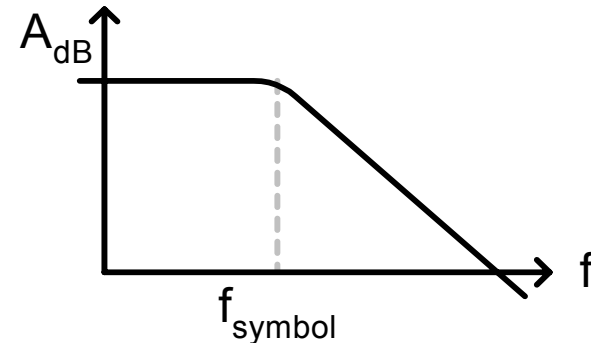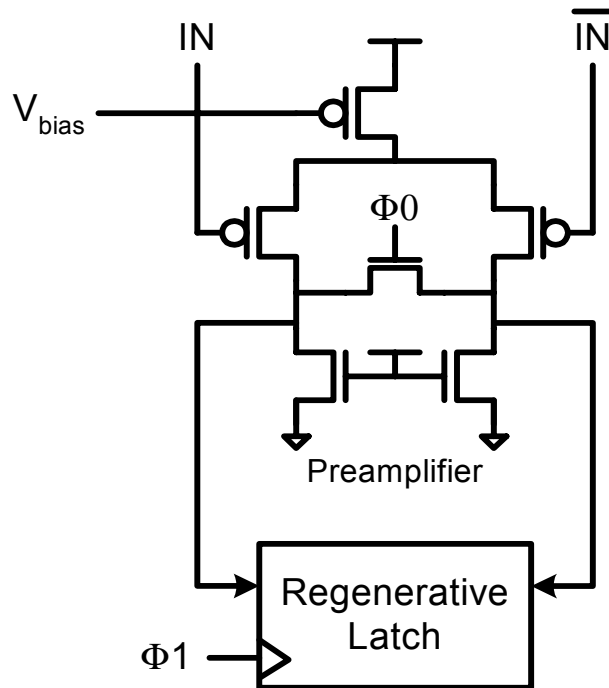
- Filter signal frequencies beyond the Nyquist rate at the receiver (helps for dealing with cross talk)
- Receiver example



- Filter's corner frequency tracks f_{symbol}


Example: Adaptive Supply Serial Links

- Jaeha Kim (Ph.D. defense 2002)

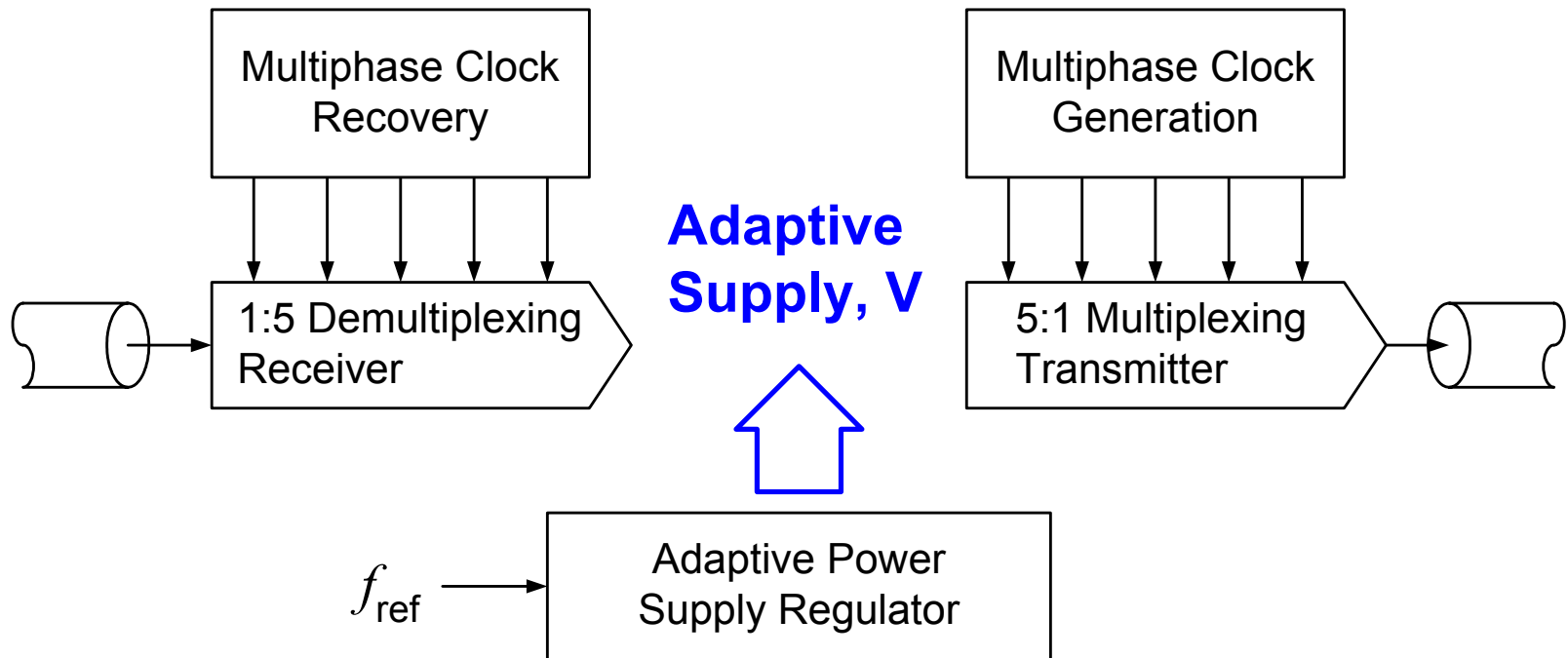


Multi-Phase Clock Generation

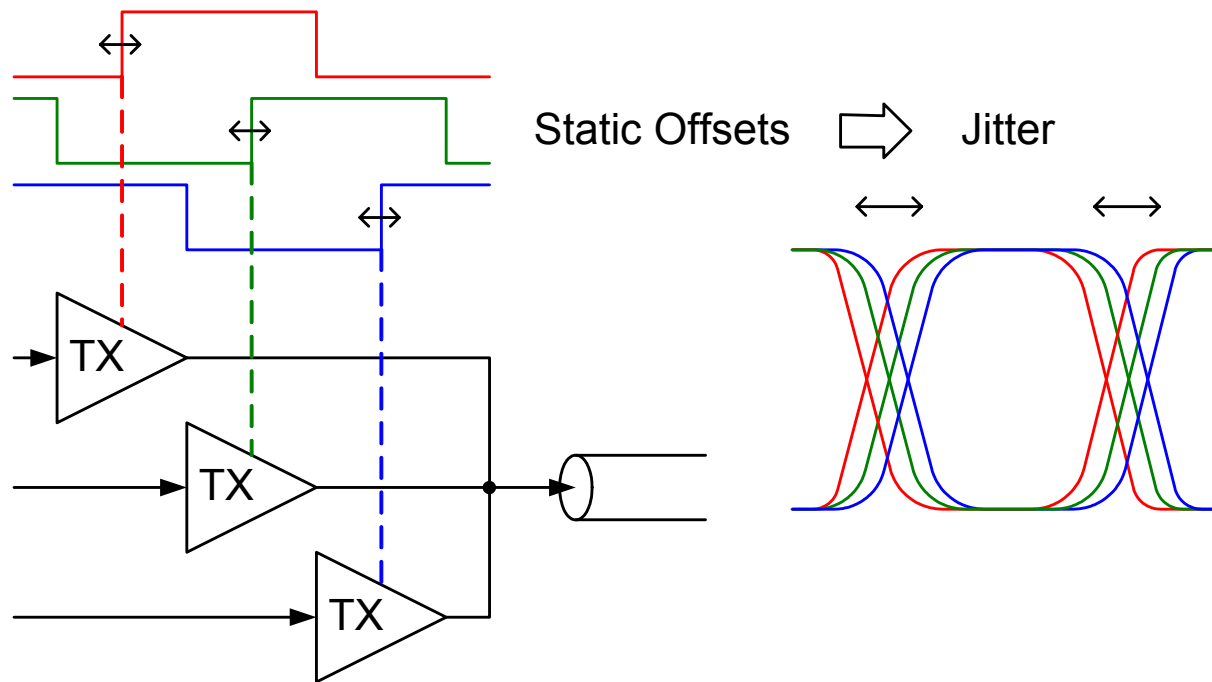- Must minimize static offsets between phases
- Generate multiphase clocks locally at each pin, but watch out for power and area overhead



Dual-Loop Clock Generation

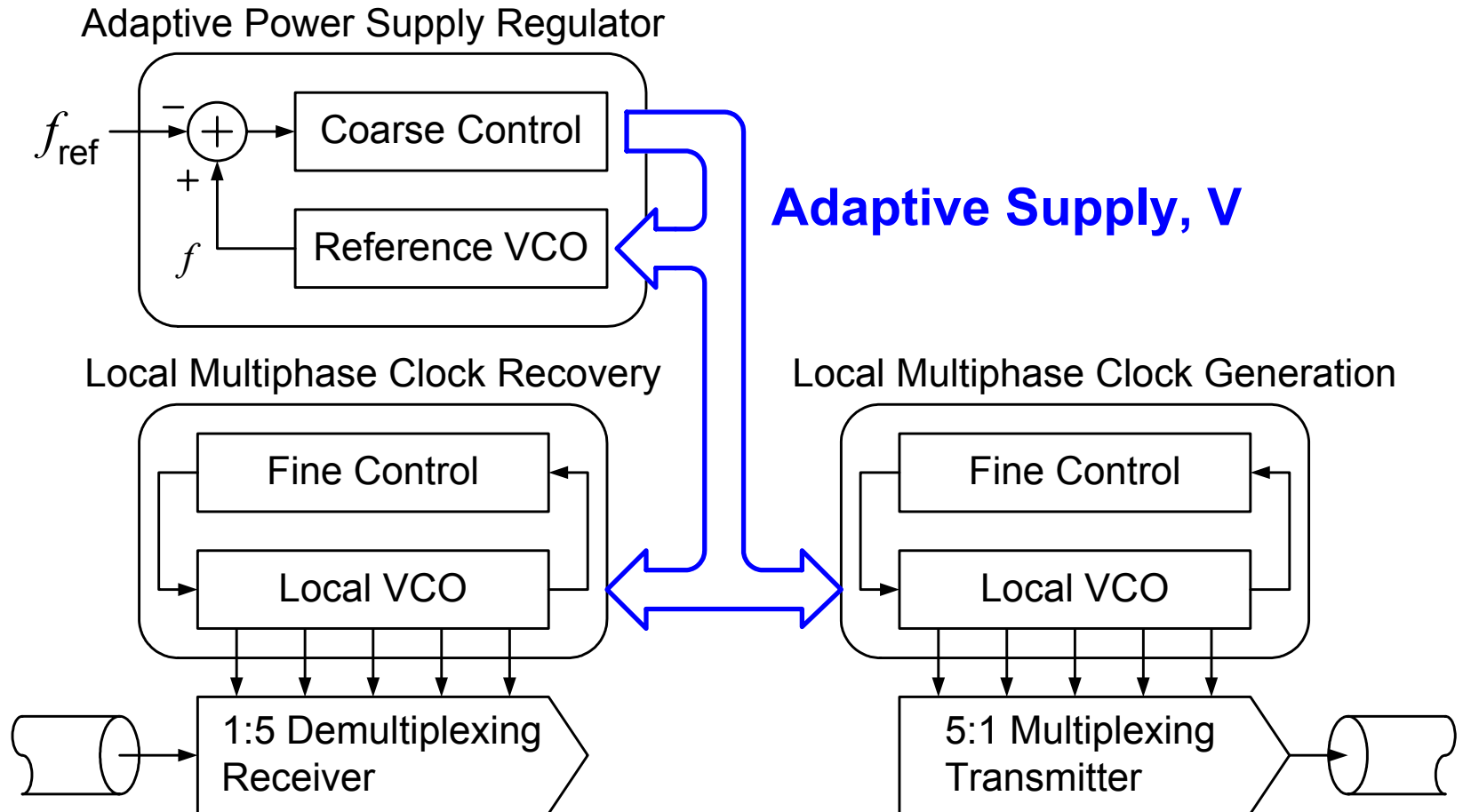


Dual-Loop Clock Generation (2)

- Global loop brings the local VCO frequency close to lock
- Narrow local tuning range ($\pm 15\%$) is sufficient to compensate for on-chip mismatches
- Narrow tuning range leads to low VCO gain
 - Small loop capacitor area (2.5pF)
 - Low sensitivity on V_{ctrl} noise


Clock Recovery

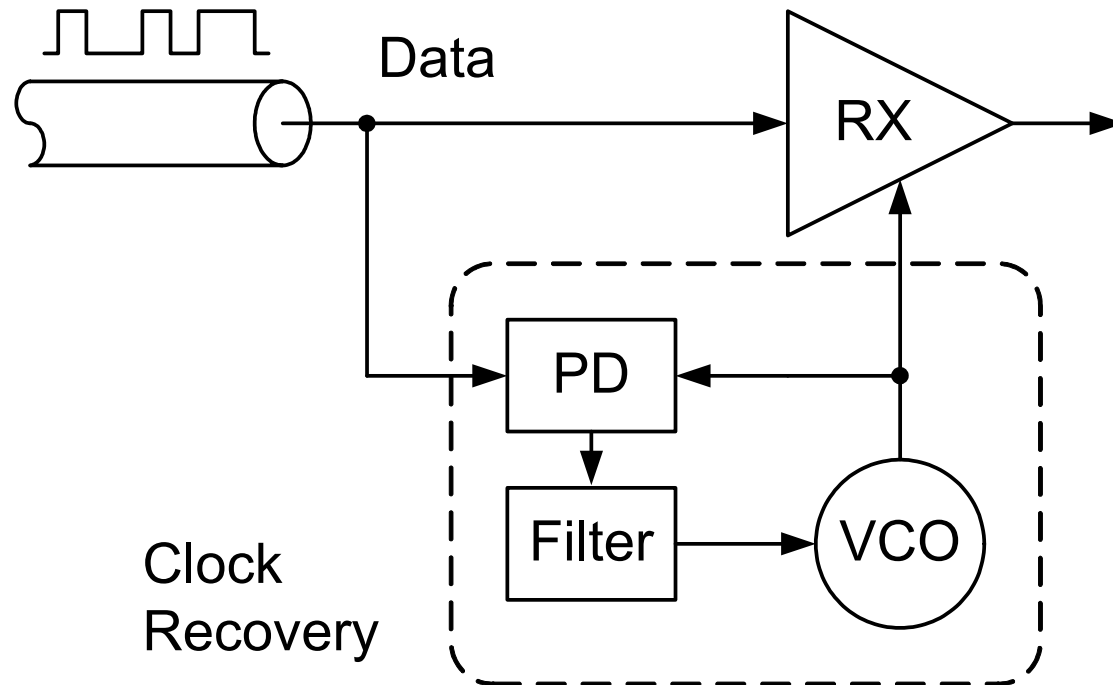- Optimal receiver timing is recovered from the incoming data stream



Phase Detection


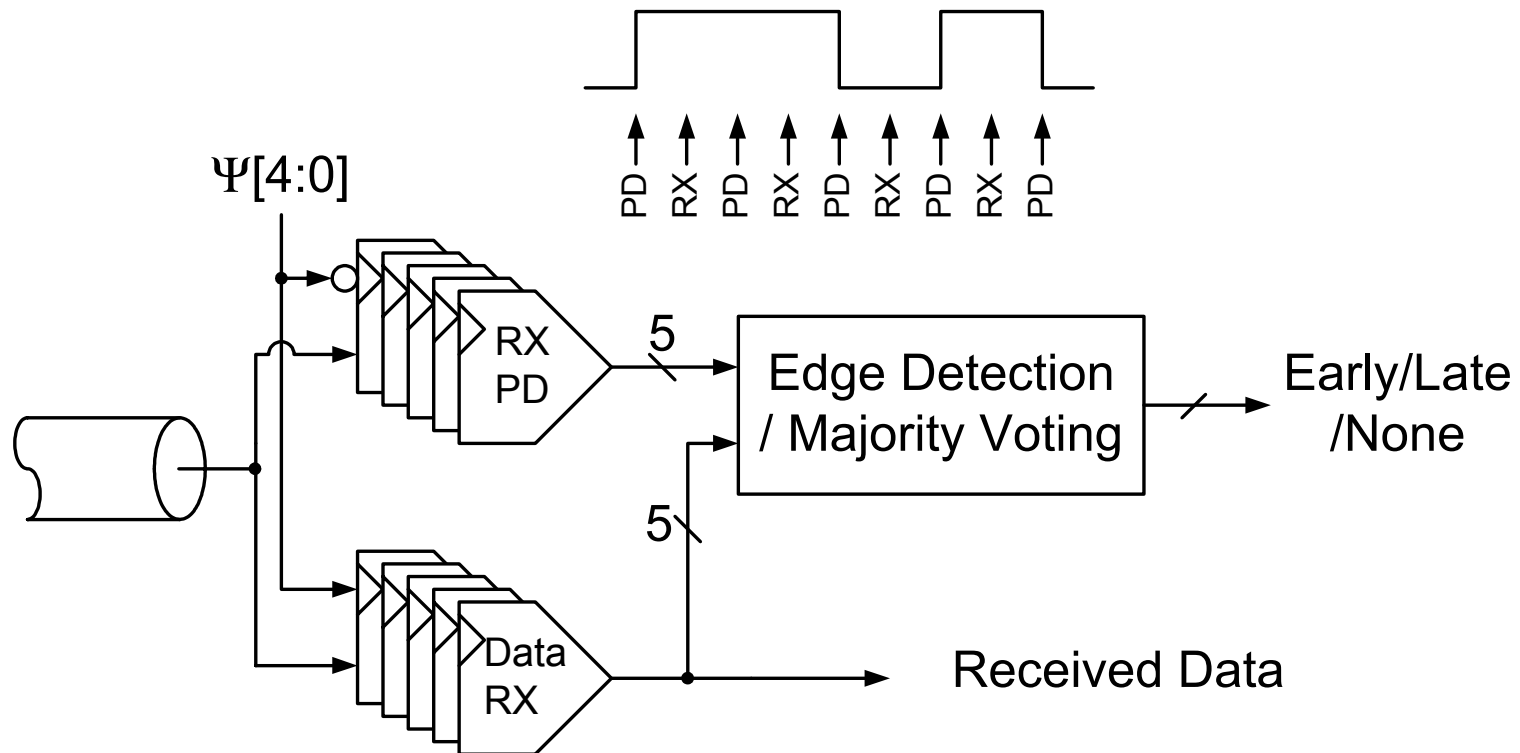
- Phase detector made of an identical set of receivers minimizes timing error




Chip Prototype

- 0.25 μ m CMOS
- 2.5V / 0.55V_{th}
- 3.1 \times 2.9mm²
- 0.4~5.0Gb/s
- 0.9~2.5V
- 5.6~375mW
- BER < 10⁻¹⁵
- Reg. Efficiency:
83-94%

Power and Performance

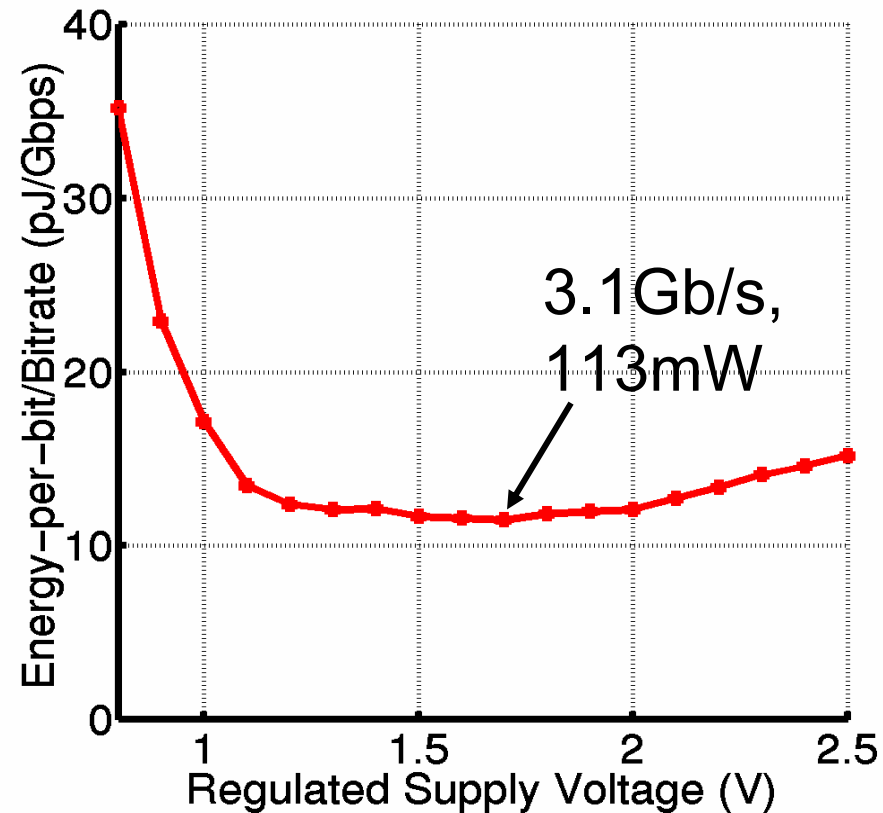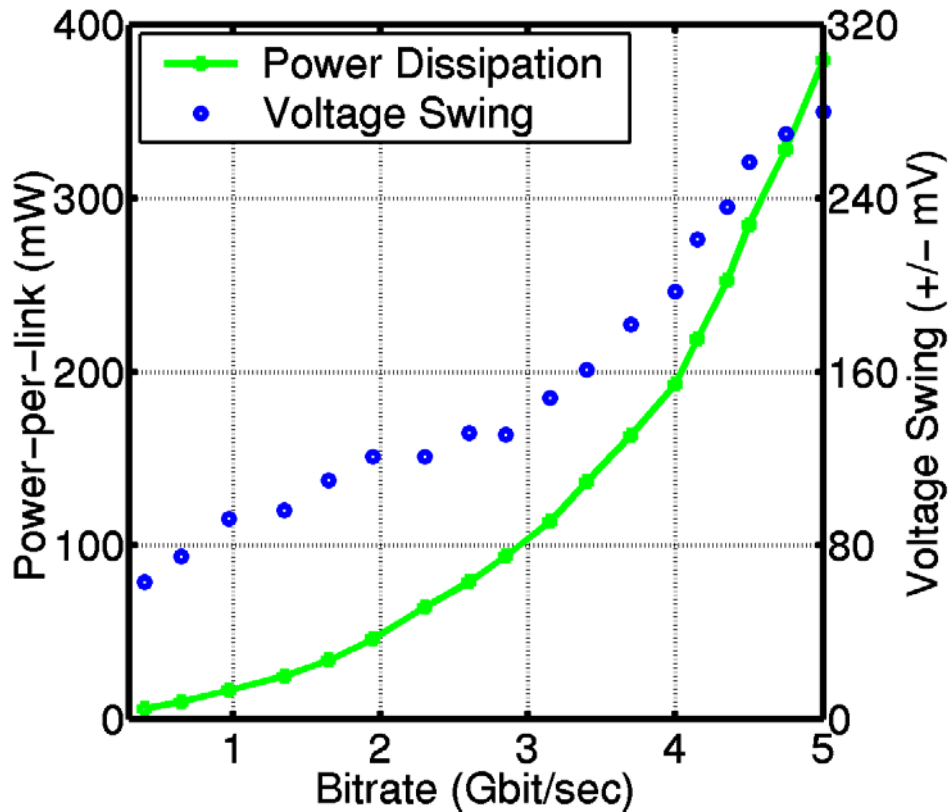

Power Breakdown

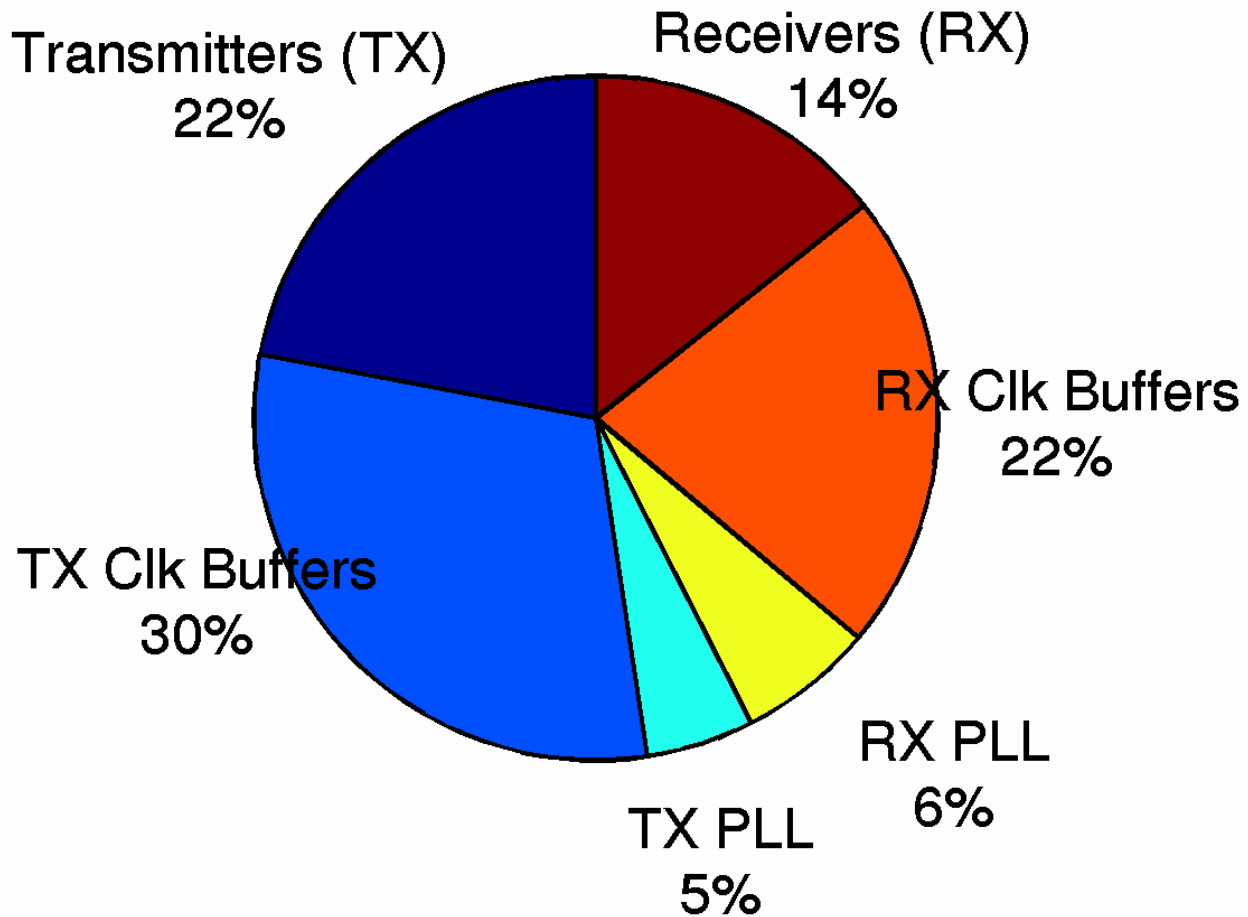

Summary

- Higher performance links require low noise → low noise solutions lead to lower power
 - Trade performance (speed) for power reduction
- DVS links enable energy-efficient link operation and also have some nice properties
- Outstanding issues with using DVS links
 - Communication during frequency and voltage transitions
 - Supply voltage regulator slew rate limits
 - Overhead of multiple regulators